

Processor Architecture II: Logic Design

Dr. Steve Goddard
goddard@cse.unl.edu

<http://cse.unl.edu/~goddard/Courses/JDEP284>

Giving credit where credit is due

- Most of slides for this lecture are based on slides created by Dr. Bryant, Carnegie Mellon University.
- I have modified them and added new slides.

2

Overview of Logic Design

Fundamental Hardware Requirements


- Communication
 - How to get values from one place to another
- Computation
- Storage

Bits are Our Friends

- Everything expressed in terms of values 0 and 1
- Communication
 - Low or high voltage on wire
- Computation
 - Compute Boolean functions
- Storage
 - Store bits of information

3


Digital Signals

 


- Use voltage thresholds to extract discrete values from continuous signal
- Simplest version: 1-bit signal
 - Either high range (1) or low range (0)
 - With guard range between them
- Not strongly affected by noise or low quality circuit elements
 - Can make circuits simple, small, and fast

4

Computing with Logic Gates

 


 - Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs
 - With some, small delay



5

Combinational Circuits

 


Acyclic Network of Logic Gates

- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs

6

Bit Equality

 

HCL Expression

```
bool eq = (a&&b) || (!a&&!b)
```


- Generate 1 if a and b are equal

Hardware Control Language (HCL)


- Very simple hardware description language
 - Boolean operations have syntax similar to C logical operations
- We'll use it to describe control logic for processors

7

Word Equality

 

Word-Level Representation

 


HCL Representation

```
bool Eq = (A == B)
```

- 32-bit word size
- HCL representation
 - Equality operation
 - Generates Boolean value

8

Bit-Level Multiplexor

 


HCL Expression

```
bool out = (s&&a) || (!s&&b)
```


- Control signal s
- Data signals a and b
- Output a when s=1, b when s=0

9

Word Multiplexor

 

Word-Level Representation

 

HCL Representation


```
int Out = [
    s : A;
    !s : B;
];
```

- Select input word A or B depending on control signal s
- HCL representation
 - Case expression
 - Series of test : value pairs
 - Output value for first successful test

10

HCL Word-Level Examples


Minimum of 3 Words

 

```
int Min3 = [
    A < B && A < C : A;
    B < A && B < C : B;
    1                : C;
];
```

- Find minimum of three input words
- HCL case expression
- Final case guarantees match

4-Way Multiplexor

 


```
int Out4 = [
    !s1&&!s0: D0;
    !s1      : D1;
    !s0      : D2;
    1        : D3;
];
```

- Select one of 4 inputs based on two control bits
- HCL case expression
- Simplify tests by assuming sequential matching

11


Arithmetic Logic Unit

 

- Combinational logic
 - Continuously responding to inputs
- Control signal selects function computed
 - Corresponding to 4 arithmetic/logical operations in Y86
- Also computes values for condition codes


12

Storing 1 Bit

 


13

Storing 1 Bit (cont.)

 


14

Physical Analogy

 


15

Storing and Accessing 1 Bit

 


16

1-Bit Latch

 

17


Transparent 1-Bit Latch

 

- When in latching mode, combinational propagation from D to Q+ and Q-
- Value latched depends on value of D as C falls


18

Edge-Triggered Latch

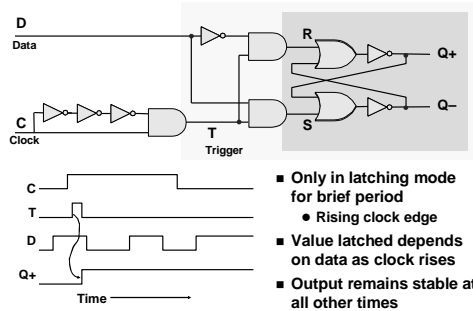

19


Registers

 

- Stores word of data
 - Different from *program registers* seen in assembly code
- Collection of edge-triggered latches
- Loads input on rising edge of clock

20



Register Operation

 

- Stores data bits
- For most of time acts as barrier between input and output
- As clock rises, loads input


21

State Machine Example

  

22


Random-Access Memory

 

- Stores multiple words of memory
 - Address input specifies which word to read or write
- Register file
 - Holds values of program registers
 - %eax, %esp, etc.
 - Register identifier serves as address
 - » ID 8 implies no read or write performed
- Multiple Ports
 - Can read and/or write multiple words in one cycle
 - » Each has separate address and data input/output

23

Register File Timing

 


Reading

- Like combinational logic
- Output data generated based on input address
 - After some delay

Writing

 - Like register
- Update only as clock rises



24

Hardware Control Language

- Very simple hardware description language
- Can only express limited aspects of hardware operation
 - Parts we want to explore and modify

Data Types

- **bool**: Boolean
 - a, b, c, ...
- **int**: words
 - A, B, C, ...
 - Does not specify word size—bytes, 32-bit words, ...

Statements

- `bool a = bool-expr ;`
- `int A = int-expr ;`

25

HCL Operations

- Classify by type of value returned

Boolean Expressions

- **Logic Operations**
 - `a && b, a || b, !a`
- **Word Comparisons**
 - `A == B, A != B, A < B, A <= B, A >= B, A > B`
- **Set Membership**
 - `A in { B, C, D }`
 - » Same as `A == B || A == C || A == D`

Word Expressions

- **Case expressions**
 - `[a : A; b : B; c : C]`
 - Evaluate test expressions a, b, c, ... in sequence
 - Return word expression A, B, C, ... for first successful test

26

Summary

Computation

- Performed by combinational logic
- Computes Boolean functions
- Continuously reacts to input changes

Storage

- **Registers**
 - Hold single words
 - Loaded as clock rises
- **Random-access memories**
 - Hold multiple words
 - Possible multiple read or write ports
 - Read word when address input changes
 - Write word as clock rises

27